
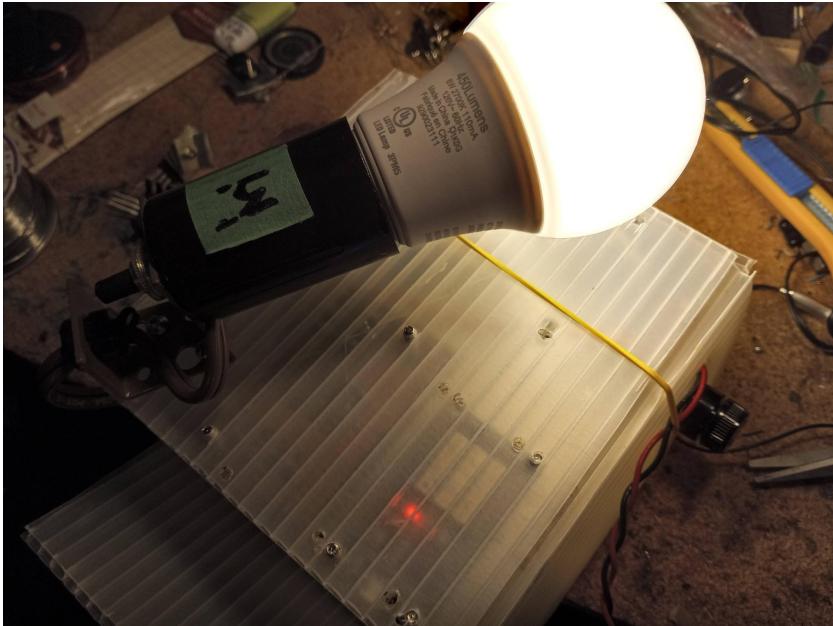


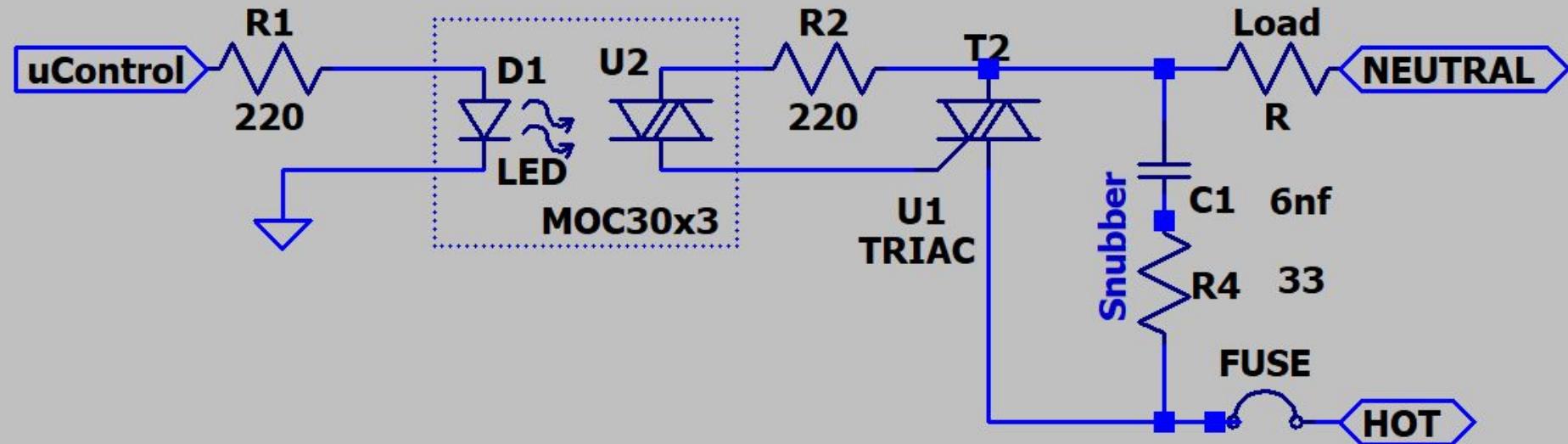AC control with Triac and uProcessor (a bigger blinky!!)



For rapid on/off cycling of AC power

Circuit diagram of triac control




Zero crossing pulse detector

R3 is for user input, and has no effect on the pulse detector.

Time from the pulse interrupt controls the triac

[Bristolwatch article](#)

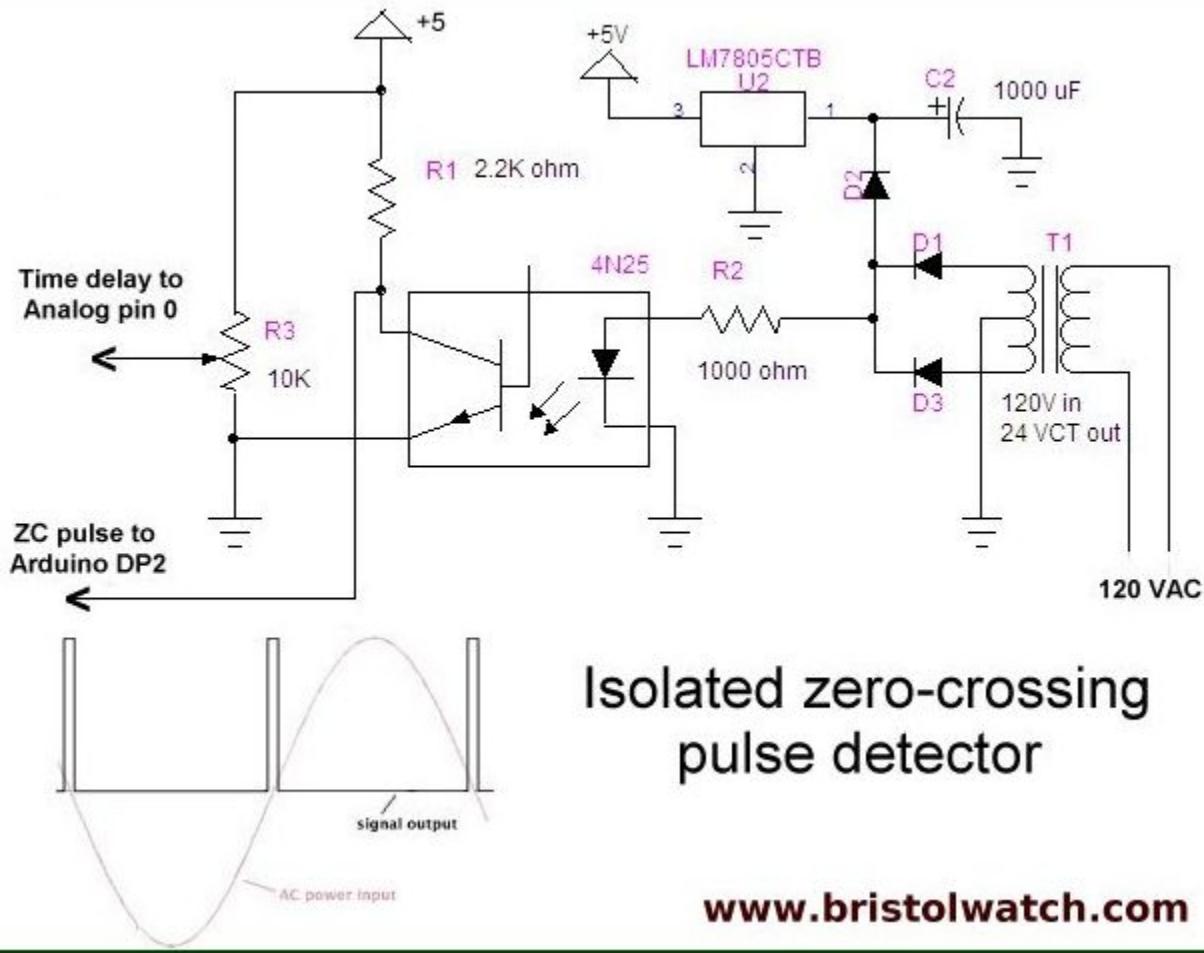

Zero crossing detector

120 Hz

3.3 v



Component layout on stripboard. Wirewrap between uController and Sense-triac board

Inside the Box

Electrical safety
tape to be applied.

A bridge rectifier
could be used
instead of messy
wiring off
the transformer

**Beware 110v AC
can kill.**



Code to Test Triac.

Uses
gpio-2
LED

```
//Purpose: to test triac operation
#define triacPulsePin 25 //out to MOC302x led
#define acOnLedPin 2 // out to on-indicator Led

void setup()  {
    pinMode(triacPulsePin, OUTPUT);
    digitalWrite(triacPulsePin, LOW);
    pinMode(acOnLedPin, OUTPUT);
    digitalWrite(acOnLedPin, LOW);
}

void loop()  {
    digitalWrite(acOnLedPin, HIGH);
    digitalWrite(triacPulsePin, HIGH);
    delay(1000); //one second
    digitalWrite(acOnLedPin, LOW);
    digitalWrite(triacPulsePin, LOW);
    delay(4000); // 4 seconds
} // end loop
```

Code that senses zero crossing

For info on interrupts, refer to Andreas Spies video <https://youtu.be/CJhWlfkf-5M>

Untested Arduino code

60 Hz AC is 16.7ms per cycle